

BRAC University

CSE250: Circuit and Electronics

Laboratory

Experiment No: 3

Name of the Experiment: Verification of KCL and KVL

Objective: This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of series circuit.

Apparatus:


- One DC Ammeter (0-1 A)
- One multimeter
- Three Resistors
- One DC power supply

Student Name: Eftykhane Rahman

Id: 18301041

Section : 20

Circuit Diagram:

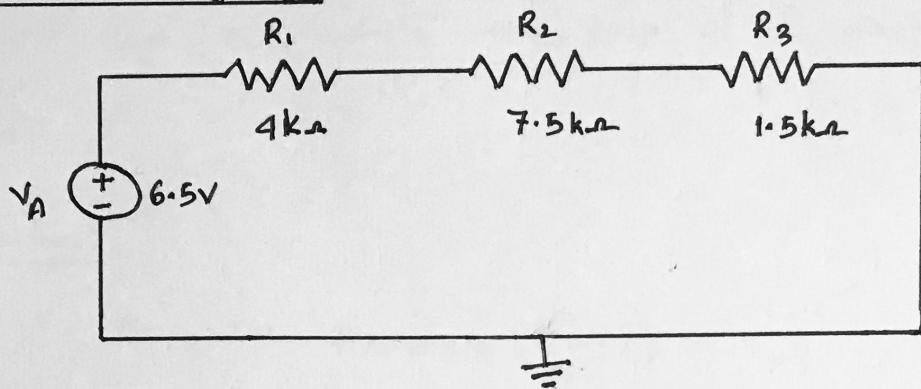

Result Analysis:

$$V_A = 6.5V, R_1 = 4k\Omega = 4 \times 10^3 \Omega, R_2 = 7.5k\Omega = 7.5 \times 10^3 \Omega$$

$$R_3 = 1.5k\Omega = 1.5 \times 10^3 \Omega$$

$$\therefore R = R_1 + R_2 + R_3 = (4 + 7.5 + 1.5) k\Omega = 13 k\Omega = 13 \times 10^3 \Omega$$

$$\therefore I = \frac{V}{R} = \frac{6.5}{13 \times 10^3} = 5 \times 10^{-4} A$$

$$\therefore V_1 = IR_1 = (5 \times 10^{-4} \times 4 \times 10^3) V = 2V$$

$$V_2 = IR_2 = (5 \times 10^{-4} \times 7.5 \times 10^3) V = 3.75V$$

$$V_3 = IR_3 = (5 \times 10^{-4} \times 1.5 \times 10^3) V = 0.75V$$

$$\therefore V = V_1 + V_2 + V_3 = (2 + 3.75 + 0.75)V = 6.5V$$

KVL Verification:


Observation	R <sub>1</sub> (kΩ)	R <sub>2</sub> (kΩ)	R <sub>3</sub> (kΩ)	V <sub>A</sub> (kV)	V <sub>1</sub> (V)	V <sub>2</sub> (V)	V <sub>3</sub> (V)	V <sub>1</sub> + V <sub>2</sub> + V <sub>3</sub> (V)
Simulation	4	7.5	1.5	6.5	2	3.75	0.75	6.5
Theoretical	4	7.5	1.5	6.5	2	3.75	0.75	6.5

Objective: This experiment is intended to verify Kirchhoff's current law (KCL) with the help of a simple parallel circuit.

Apparatus:

- One DC Ammeter (0 - 1 A)
- Three resistors
- One multimeter
- One DC supply

Circuit Diagram:

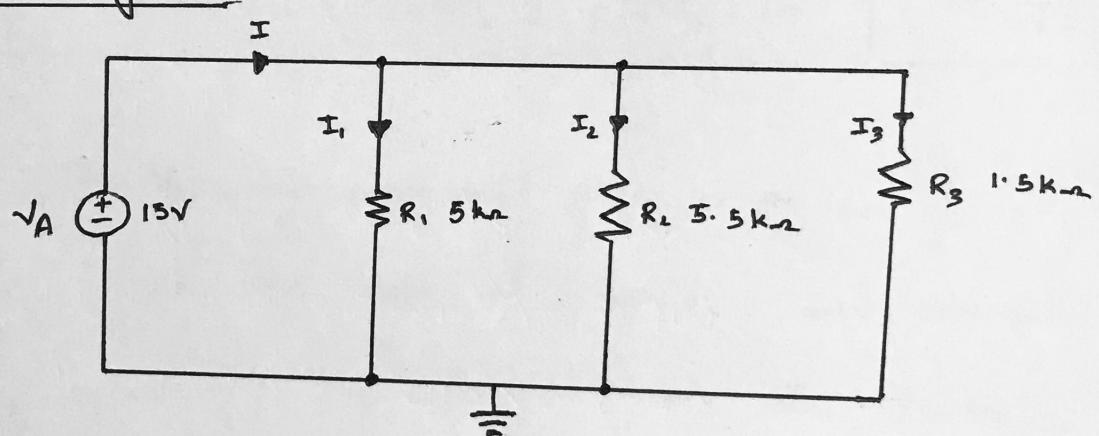

Result Analysis:  $V_A = 15V$ ,  $R_1 = 5\text{ k}\Omega$ ,  $R_2 = 5.5\text{ k}\Omega$

$$R_3 = 1.5\text{ k}\Omega$$

$$\therefore R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{5} + \frac{1}{5.5} + \frac{1}{1.5}} = 0.95\text{ k}\Omega$$

$$\therefore I = \frac{V}{R} = \frac{15}{0.95 \times 10^3} = 15.73\text{ mA}$$

$$\therefore I_1 = \frac{V}{R_1} = \frac{15}{5 \times 10^3} = 3 \text{ mA}$$

$$\therefore I_2 = \frac{V}{R_2} = \frac{15}{5.5 \times 10^3} = 2.73 \text{ mA}$$

$$\therefore I_3 = \frac{V}{R_3} = \frac{15}{1.5 \times 10^3} = 10 \text{ mA}$$

$$\therefore I = I_1 + I_2 + I_3 : (3 + 2.73 + 10) \text{ mA} = 15.73 \text{ mA}$$

### KCL Verification:

Observation	$R_1$ (k $\Omega$ )	$R_2$ (k $\Omega$ )	$R_3$ (k $\Omega$ )	$I$ (mA)	$I_1$ (mA)	$I_2$ (mA)	$I_3$ (mA)	$I_1 + I_2 + I_3$ (mA)
Simulation	5	5.5	1.5	15.73	3	2.73	10	15.73
Theoretical	5	5.5	1.5	15.73	3	2.73	10	15.73

Discussion: The following experiment gives us the idea of KVL and KCL with the help of series and parallel circuits accordingly. The experiment was done flawlessly and the values got from pSpice software simulation and theoretically was same. So it can be said that it was a successful experiment and the challenges were overcome so technically.

